

Experiment - 4

Operational Amplifier Circuits

NAME - ANINDYA V, JAYVARGEE YA

ROLL NO. - 200101015

INDIAN INSTITUTE OF TECHNOLOGY GUWAHATI

Department of Electronics & Electrical Engineering

EE102: Basic Electronics Laboratory

Expt.No. 4: Operational Amplifier Circuits

Objectives:

1. To study the comparator circuit realized using an Op-Amp.
2. To study inverting and non-inverting amplifier circuits realized using an Op-Amp.
3. To study a practical integrator circuit realized using an Op-Amp.

Materials Required:


1. Equipment: Breadboard, Function Generator, Oscilloscope, DC Power Supply
2. Components: LM741 Op Amp (One), 10k Ω (Two), 39k Ω (One), 68k Ω (One), 100k Ω (One), 2.2nF (One)

Precautions and Guidelines:


1. The Op-Amp generally works on split power supply (e.g. ± 12 V). Both positive and negative power supplies must be present whenever op-amp is powered.
2. The range of power supply is from ± 5 V to ± 15 V. Do not forget to connect the common terminal of the power supply to the ground on the breadboard.
3. The Op-Amp will not function properly if only one side of power supply is connected or positive and negative power supplies are interchanged.

Pre-Lab Work:

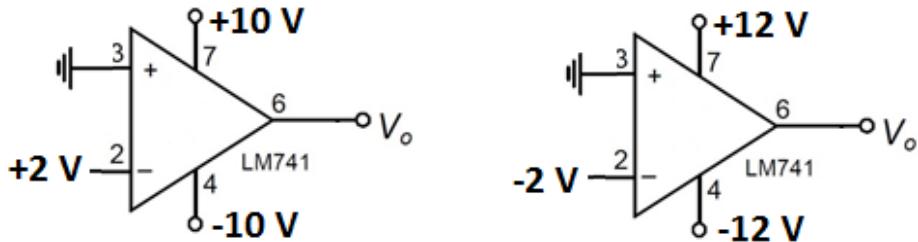1. For the op-amp circuits given below, predict the ideal outputs in each case.



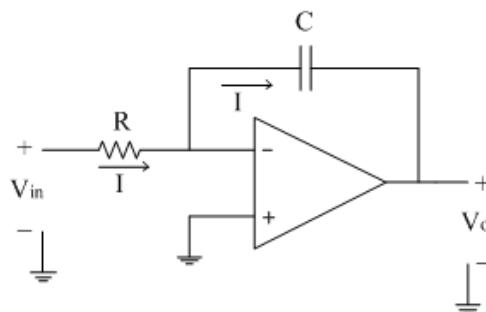2. Derive the input-output relationship (V_o/V_i) for the circuit in Part B.
3. Derive the input-output relationship (V_o/V_i) for the circuit in Part C.
4. For the ideal integrator circuit shown below, derive the input-output relationship (V_o/V_{in}).



Part A: Comparator

- Assemble the circuit as shown in Fig.1. Set the DC power supply voltage to ± 12 V. Make sure that the DC power supply ground is connected to the circuit ground.
- Apply a $500 \text{ mV}_{\text{p-p}}$, 500 Hz sine wave as input (V_i) from the function generator. Connect Ch1 of the oscilloscope to V_i and Ch2 to output (V_o).
- Observe V_o and V_i and note down the peak-to-peak value of V_o .
- Now, change the DC power supply voltage values to ± 10 V and ± 14 V. Note down the peak-to-peak values of V_o for each case.

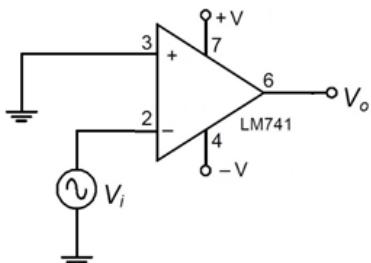


Fig. 1

DC Supply (in Volt)	Peak-to-peak of V_o (in Volt)
± 12	
± 10	
± 14	

Part B: Inverting Amplifier

- Assemble the circuit shown in Fig.2 with $R_1 = 100 \text{ k}\Omega$ and $R_2 = 10 \text{ k}\Omega$. Set the DC power supply voltage to ± 12 V. Make sure the power supply ground is connected to the circuit ground.
- Apply a $200 \text{ mV}_{\text{p-p}}$, 1 kHz sine wave at V_i from the function generator and see the output V_o .
- Observe V_o and V_i , and determine the voltage gain of Op-Amp, $A = V_o/V_i$.
- Change R_1 to $10 \text{ k}\Omega$, $39 \text{ k}\Omega$ and $68 \text{ k}\Omega$ and find the voltage gain for each case.

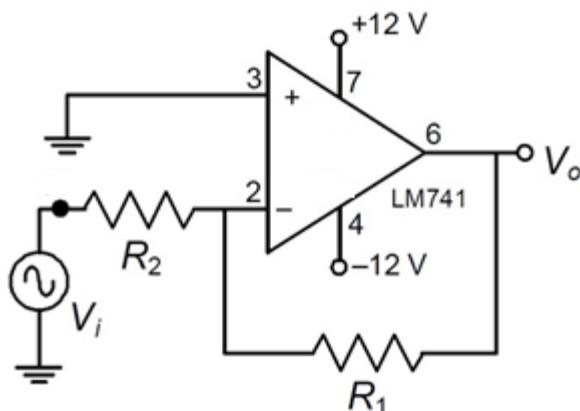


Fig. 2

Part C: Non-Inverting Amplifier

- Assemble the circuit shown in Fig.3 with $R_1 = 100 \text{ k}\Omega$ and $R_2 = 10 \text{ k}\Omega$. Set the DC power supply voltage to ± 12 V. Make sure the power supply ground is connected to the circuit ground.
- Apply a $200 \text{ mV}_{\text{p-p}}$, 1 kHz sine wave at V_i from the function generator and see the output V_o .
- Observe V_o and V_i , and determine the voltage gain of Op-Amp, $A = V_o/V_i$.
- Change R_1 to $10 \text{ k}\Omega$, $39 \text{ k}\Omega$ and $68 \text{ k}\Omega$ and find the voltage gain for each case.

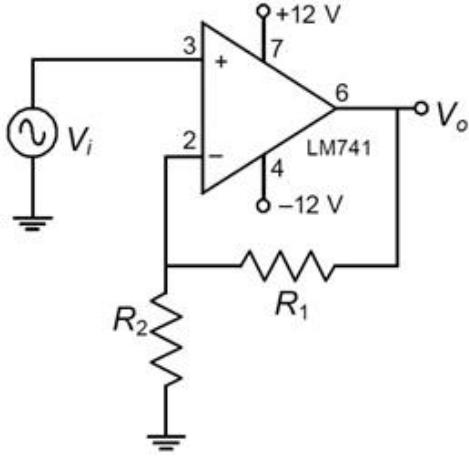


Fig.3

Part D: Practical Integrator

An ideal integrator suffers from two main limitations:

- The output of the integrator is inversely proportional to the time constant $\tau = RC$. The larger the time constant τ , the longer it takes to saturate the integrator.
- The second limitation is the presence of offset voltage even for zero input. It may be only a few millivolts, but it gets integrated over time and eventually drives the Op-Amp output to saturation. To prevent this from occurring, a large resistor is added in parallel with the capacitor.

- Assemble the circuit shown in Fig.4. Set the DC power supply voltage to ± 12 V. Make sure the power supply ground is connected to the circuit ground.
- Apply a $1 \text{ V}_{\text{p-p}}, 10 \text{ kHz}$ square wave at V_i from the function generator.
- Connect Ch1 of oscilloscope to the input (V_i) and Ch2 to the output (V_o) of the circuit.
- Set the time base of the oscilloscope to $20 \mu\text{s}/\text{div}$ and voltage scales of each channel to $500 \text{ mV}/\text{div}$.
- Observe the waveforms and sketch V_i and V_o , one below the other with identical time and amplitude axes.

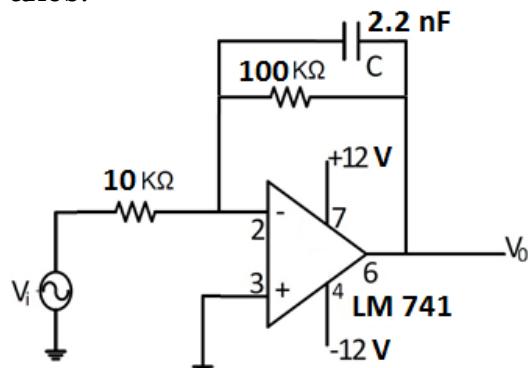


Fig.4

Part D: Lab Report

Prepare and submit a lab report as specified in the general instructions regarding the lab. Include the answers to the following questions in the report:

- For a source with high internal impedance which configuration (inverting or non-inverting) will be suitable for designing a good amplifier?

Prelab 4

200101015

Anindya Vijayvargiya

Ans1

Given Since in the first circuit $V_+ < V_-$

$$V_o = -V_{cc} = -10V$$

in the second circuit $V_+ > V_-$

$$V_o = +V_{cc} = 12V$$

Ans2

$$V_2 \approx V_3 = 0$$

applying KCL at node 2,

$$\frac{V_i - V_2}{R_2} = \frac{V_2 - V_o}{R_1} \quad (\text{As } V_2 = 0)$$

$$\boxed{\frac{V_o}{V_i} = -\frac{R_1}{R_2}}$$

Ans 3

$$V_2 \approx V_3 = V_i$$

applying KCL at node 2

$$\frac{V_i - 0}{R_2} = \frac{V_o - V_i}{R_1}$$

$$\left| \frac{V_o}{V_i} = \left(1 + \frac{R_1}{R_2} \right) \right.$$

Ans 4

$$V_- \approx V_+ = 0$$

applying ~~KCL~~ KVL,

$$V_{in} - IR - \frac{1}{C} \int I dt = V_o$$

$$\text{Since } V_- = 0, \quad I = \frac{V_{in}}{R}$$


$$\left| V_o = -\frac{1}{RC} \int V_{in} dt \right|$$

Observations


Part A:

DC Supply (in Volt)	P-P V _o (in Volt)
±12	21.92
±10	17.70
±14	26.00


12V

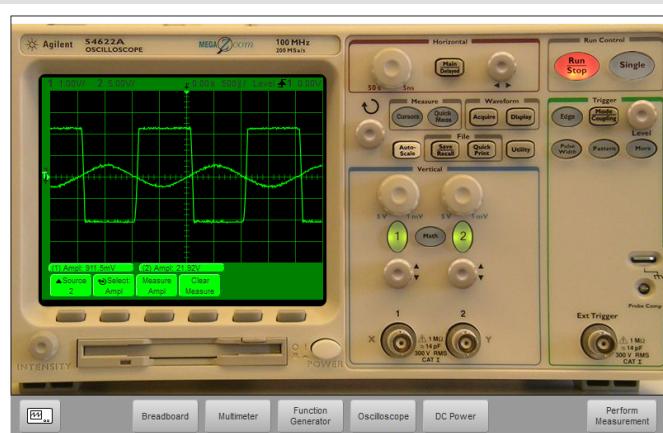

10V

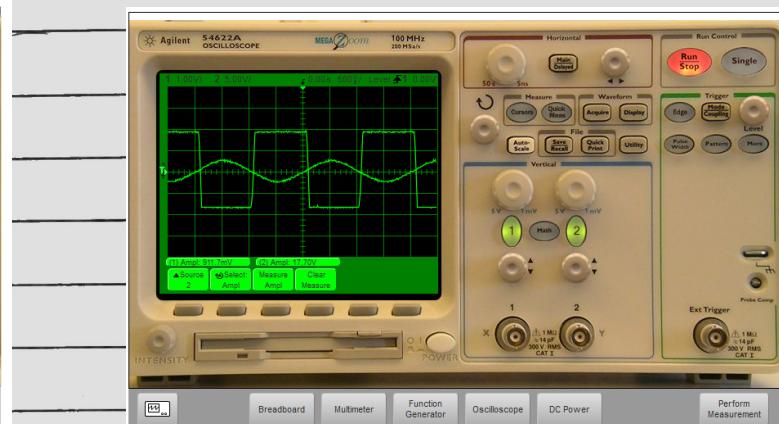

14V

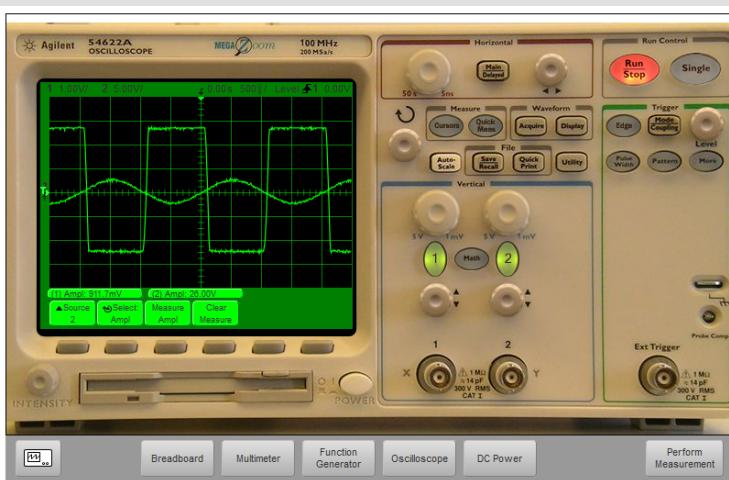

Part B:

Value of R_i
(in Ω)

V_i
(in Volts)

V_o

Voltage gain
(V_o/V_i)

100k

399.5m

3.802

- 9.516

10k

395.0m

392.1m

- 0.993

39k

369.8m

1.5668

- 4.234

68k



388.0m

2.790

- 7.195



100k

10k

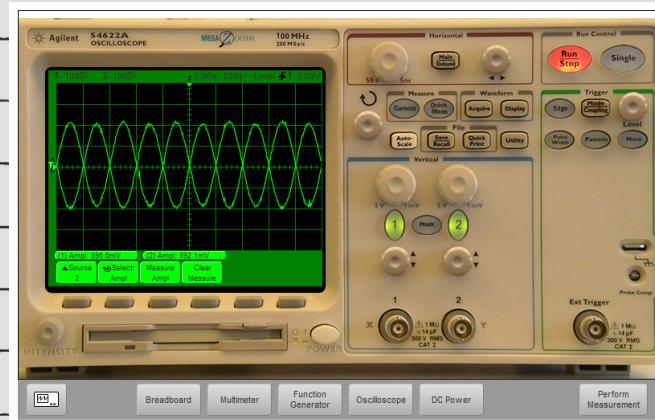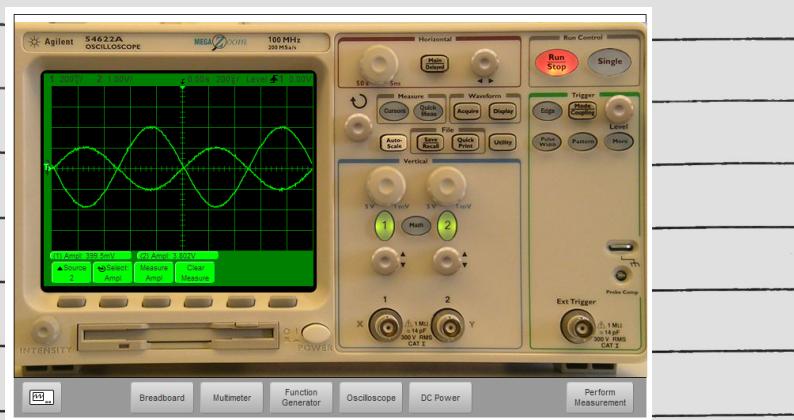

39k

68k

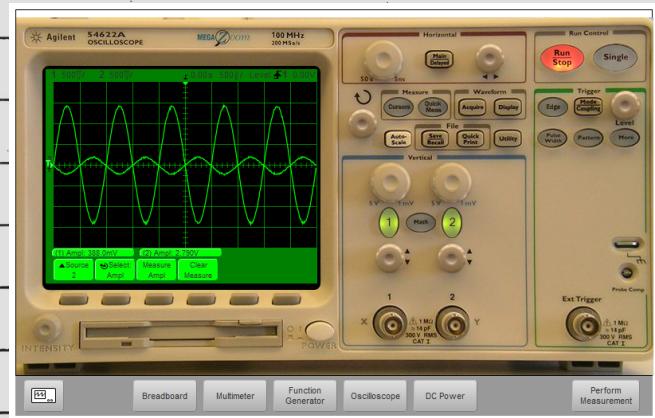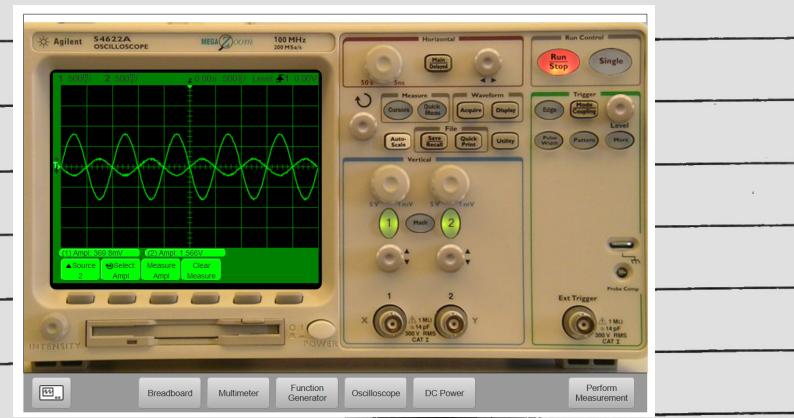


Part C:


Value of R_i (in Ω)	V_i (in Volt)	V_o (in Volt)	Voltage gain (V_o/V_i)
----------------------------------	--------------------	--------------------	-------------------------------

100k	369.8m	4.180	11.303
10k	398.5m	797.2m	2.001
39k	392.6m	1.999	5.092
68k	399.4m	3.187	7.979


100k

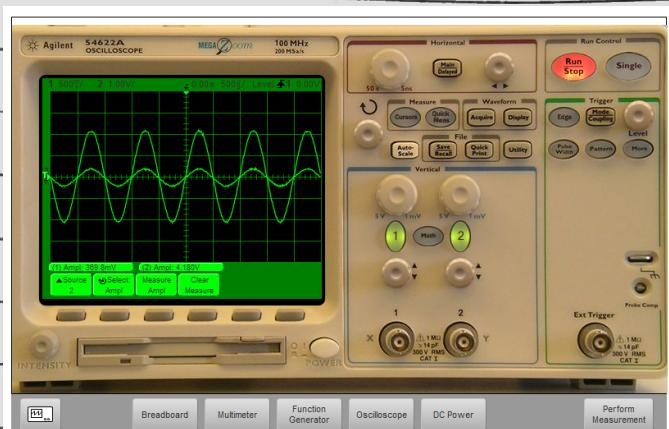


10k

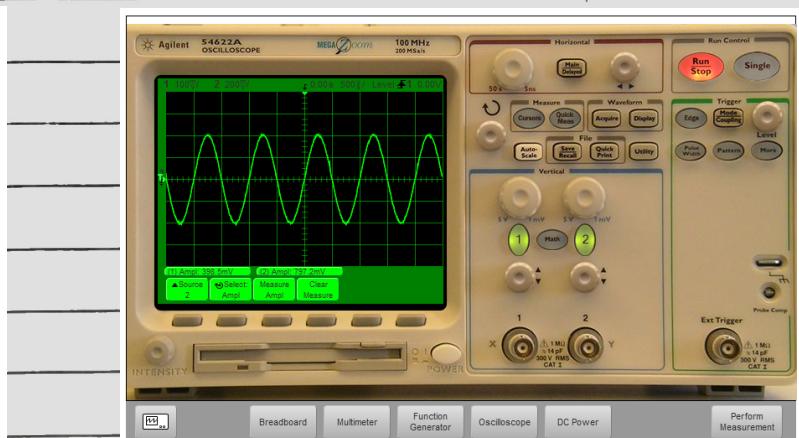



39k

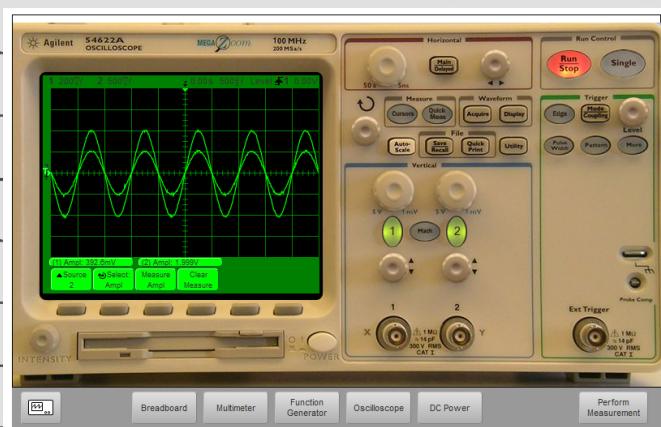

68k

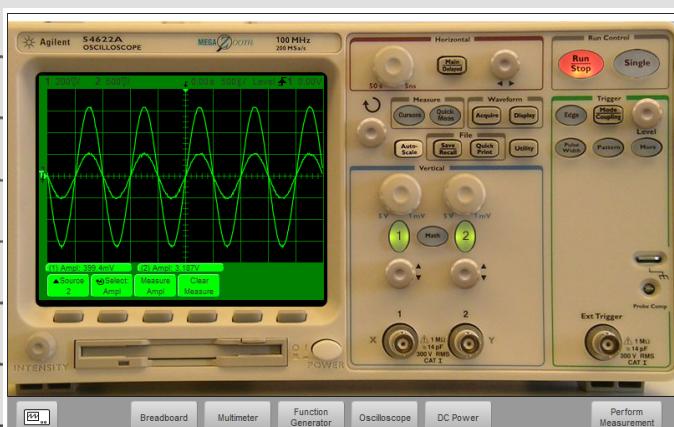


Part D:

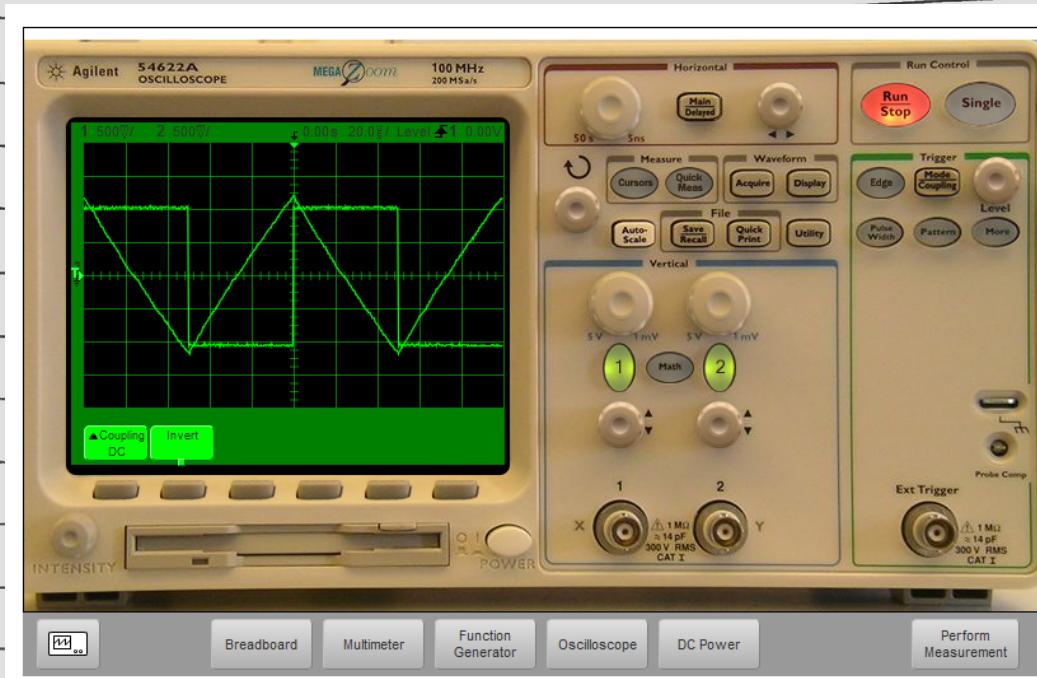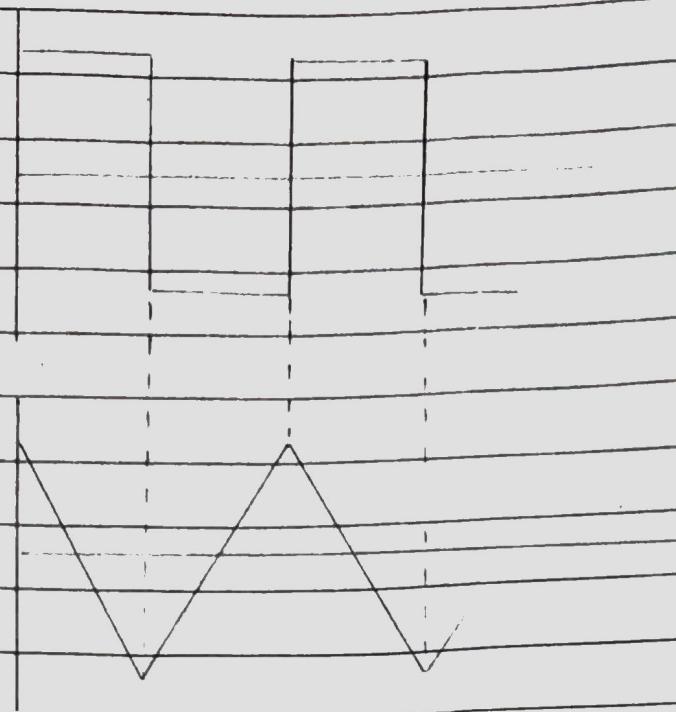

Answers

To obtain a good amplifier circuit it would be better to use non-inverting configurations, as:

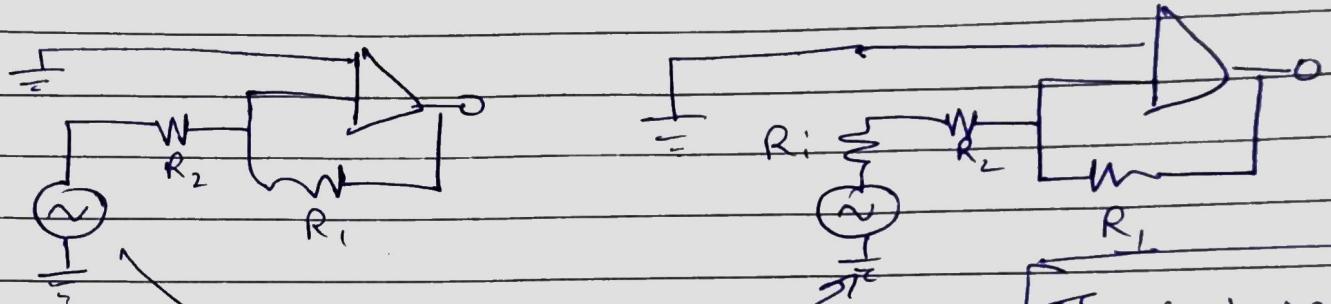- having high internal impedance in inverting configuration would mean ~~adding to the~~ increasing value of R_2 and thus decreasing the ~~voltage~~ gain ($V_{O/I} = -\frac{R_1}{R_2}$).



Source with internal impedance
can be replaced with ideal source with ext. impedance

Thus, here ~~R_1~~

$$\frac{V_O}{V_I} = -\frac{R_1}{R_2 + R_s}$$

- having high internal impedance in non-inverting configuration would not change the voltage gain at all

